

ECE 341: JUNIOR DESIGN

Accelerated Project Microphone Design

Written by Mark Ellarma

Date: February 27, 2021

1 Schematic

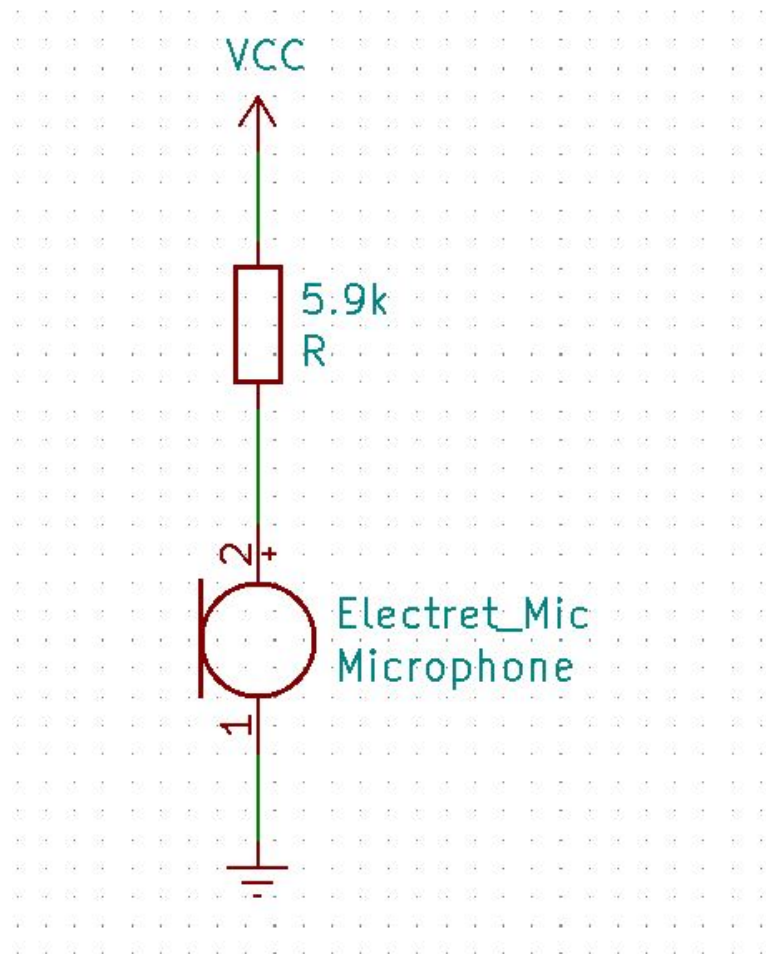


Figure 1: Microphone Schematic

2 Datasheet

SPECIFICATIONS

directivity	omnidirectional	
sensitivity (S)	-42 \pm 3 dB	f = 1KHz, 1Pa 0dB = 1V/Pa
sensitivity reduction (Δ S-Vs)	-3 dB	f = 1KHz, 1Pa Vs = 2.0 ~ 1.5 V dc
operating voltage	2 V dc (standard), 10 V dc (max.)	
output impedance (Zout)	2.2 K Ω	f = 1KHz, 1Pa
operating frequency (f)	100 ~ 20,000 Hz	
current consumption (Idss)	0.5 mA max.	Vs = 2.0 V dc RL = 2.2K Ω
signal to noise ratio (S/N)	56 dBA	f = 1KHz, 1Pa A-weighted
operating temperature	-20 ~ +70° C	
storage temperature	-20 ~ +70° C	
dimensions	ϕ 6.0 x 5.0 mm	
weight	0.30 g max.	
material	Al	
terminal	pin type (Au plating, hand soldering only)	
RoHS	yes	

Figure 2: Microphone Specifications

3 Calculations

1. Convert the sensitivity to volts per Pascal

$$10^{\frac{-42 \text{ dB}}{20}} = \boxed{7.943 \frac{\text{mV}}{\text{Pa}}}$$

2. Convert volts per Pascal to current per Pascal

$$\frac{7.943 \frac{\text{mV}}{\text{Pa}}}{2.2 \text{ k}\Omega} = \boxed{3.611 \frac{\mu\text{A}}{\text{Pa}}}$$

3. Max output current occurs at max pressure 2 Pa.

$$I_{max} = 2 \text{ Pa} * 3.611 \frac{\mu\text{A}}{\text{Pa}} = \boxed{7.221 \mu\text{A}}$$

4. Calculate bias resistor. In the following equation, V_{mic} is microphone standard operating voltage.

$$R = \frac{V_{cc} - V_{mic}}{I_S} = \frac{5 \text{ V} - 2 \text{ V}}{0.5 \text{ A}} = 6 \text{ k}\Omega \approx \boxed{5.9 \text{ k}\Omega}$$